

# PP Capacitors Inductors 004

Unlimited Attempts.

The current through a 400 nF capacitor is  $0.05e^{-\frac{t}{2 \mu s}}$  A. The voltage across the capacitor at time  $t = 0$  is 1 V.

What is the voltage  $v$  across the capacitor at time  $t = \infty$ ?

Given Variables:

...

Calculate the following:

$v$  (V) :

1.25



Hint: Check the units