PP Nodal Mesh 015
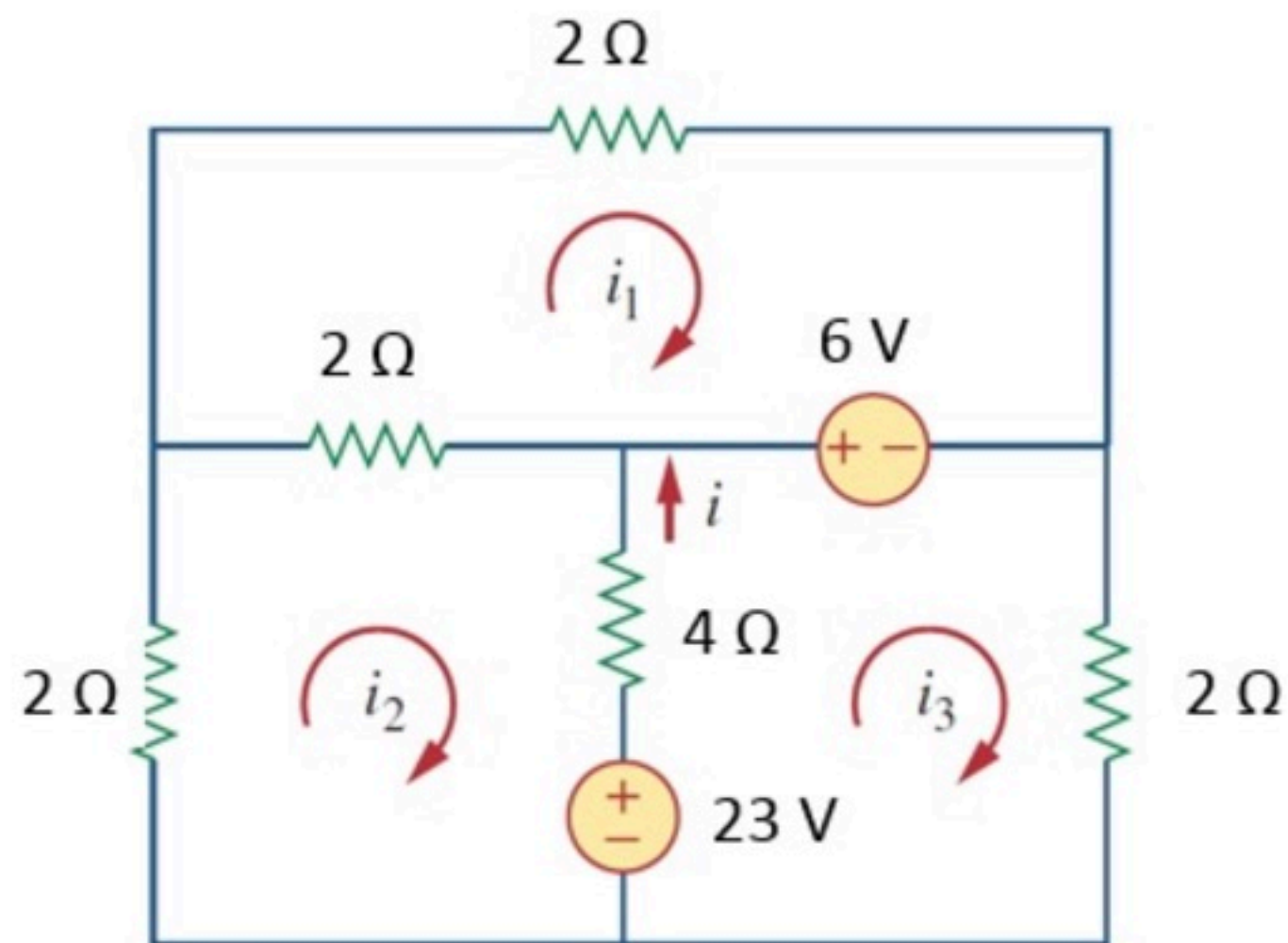
Find the current i. Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.

Given Variables:

. : . .

Calculate the following:

i (A) :

3.5 ✓

___

Hint: Mind the direction of the sources