## Lecture 8

Eigenfunctions and differential equations

Fourier series


#### UC San Diego

#### Preview of today's lecture

◆ Fourier series

- Orthogonality and computing the Fourier series
- ◆ Most important example: the rectangular pulse train

### Eigenfunctions of a LTI system

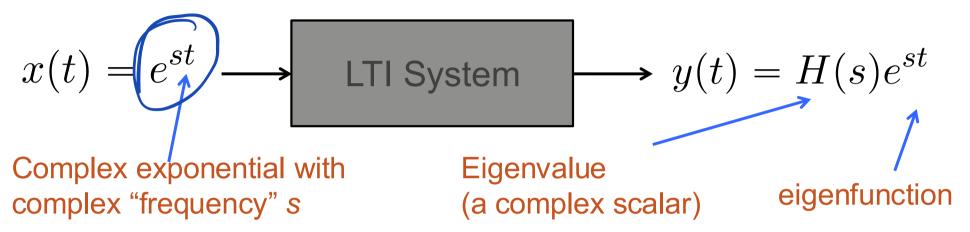

- ◆ CT complex exponentials are eigenfunctions of LTI systems
  - igspace Attenuated and scaled according to H(s) (system response)
  - → The system response is Laplace transform of the impulse response
  - → Will be studied in other courses like ECE 101

#### Special case of complex sinusoids

◆ Frequency response is used to characterize LTI systems

$$e^{j\omega t} \longrightarrow h(t) \longrightarrow H(j\omega)e^{j\omega t}$$

◆ The frequency response is computed from the impulse response

$$H(j\omega) = \int_{-\infty}^{\infty} h(t)e^{-j\omega t}dt$$

◆ This is the <u>Fourier transform</u> of the impulse response of the system

## Frequency response for a LCCDE july 4T

◆ Consider a system where the input and output are related by a linear constant coefficient differential equation


$$\sum_{k=0}^{N} a_k \frac{d^k y(t)}{dt^k} = \sum_{k=0}^{M} b_k \frac{d^k x(t)}{dt^k}$$

◆ The frequency response has a special form

$$H(j\omega) = \frac{\sum_{k=0}^{M} b_k(j\omega)^k}{\sum_{k=0}^{N} a_k(j\omega)^k}$$
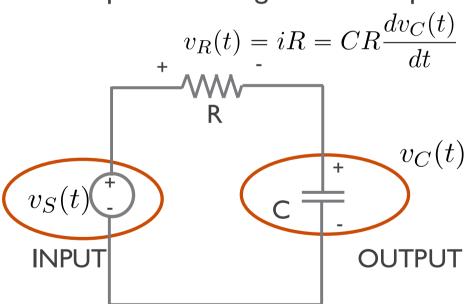
### RLC circuits are modeled with differential equations

- ◆ Recall this RC lowpass filter
  - → Source voltage as the input
  - → Capacitor voltage as the output



Example

Current through capacitor

$$i = C \frac{dv_C(t)}{dt}$$

Resulting differential equation

$$RC\frac{dv_C(t)}{dt} + v_C(t) = v_S(t)$$

### Frequency response of the circuit

- ◆ RLC circuits that are "at rest" are LTI (they have zero initial conditions, no stored charge, no memory)
- lacktriangle Consider the differential equation with input  $v_S(t)$  and output  $v_C(t)$

$$RC\frac{dv_C(t)}{dt} + v_C(t) = v_S(t)$$

◆ The frequency response is

$$H(j\omega) = \frac{1}{RCj\omega + 1}$$

lacktriangledown If  $v_S(t)=e^{j\omega t}$  then  $v_C(t)=H(j\omega)e^{j\omega t}$ 

### Response for the negative frequency

lacktriangle Continuing the same example with input  $v_S(t)$  and output  $v_C(t)$ 

$$RC\frac{dv_C(t)}{dt} + v_C(t) = v_S(t)$$
  $H(j\omega) = \frac{1}{RCj\omega + 1}$ 

lacktriangle If we input  $v_S(t)=e^{-j\omega t}$  then

$$v_C(t) = H(-j\omega)e^{-j\omega t}$$

### Some simplifications

Observe that

$$H(-j\omega) = \frac{1}{-RCj\omega + 1}$$

◆ But observe the

$$H^*(j\omega) = \frac{1}{(RCj\omega + 1)^*}$$
$$= \frac{1}{-RCj\omega + 1}$$
$$= H(-j\omega)$$

This is an example of conjugate symmetry

### Inputting a cosine 1/2

♦ Now excite the circuit by a real cosine signal

$$v_S(t) = A\cos(\omega t + \theta)$$
$$= \frac{1}{2}Ae^{j\theta}e^{j\omega t} + \frac{1}{2}Ae^{-j\theta}e^{-j\omega t}$$

Because the system is LTI

$$v_C(t) = \frac{1}{2} A e^{j\theta} H(j\omega) e^{j\omega t} + \frac{1}{2} H(-j\omega) A e^{-j\theta} e^{-j\omega t}$$

Because of conjugate symmetry

### Inputting a cosine 2/2

◆ Because of conjugate symmetry

$$v_C(t) = \frac{1}{2} A e^{j\theta} H(j\omega) e^{j\omega t} + \frac{1}{2} H^*(j\omega) A e^{-j\theta} e^{-j\omega t}$$
$$= 2 \operatorname{Re} \left[ \frac{1}{2} A e^{j\theta} H(j\omega) e^{j\omega t} \right]$$

Simplifying

$$v_C(t) = A|H(j\omega)|\operatorname{Re}\left[e^{j\theta}e^{j\angle H(j\omega)}e^{j\omega t}\right]$$
$$= A|H(j\omega)|\cos(\omega t + \theta + \angle H(j\omega))$$

## See the connection to phasors

$$RC\frac{dv_C(t)}{dt} + v_C(t) = v_S(t)$$

◆ Consider a cosine input

$$v_S(t) = A\cos(\omega t + \theta)$$
$$= \operatorname{Re}\left[Ae^{j\theta}e^{j\omega t}\right]$$

Solve the problem with phasors

$$\mathbf{V}_S = Ae^{j\theta}$$

KVL 
$$RCj\omega \mathbf{V}_C + \mathbf{V}_C = \mathbf{V}_S$$
  $\mathbf{V}_C = \frac{1}{RCj\omega + 1}\mathbf{V}_S$ 



$$\mathbf{V}_C = \frac{1}{RCi\omega + 1}\mathbf{V}_S$$

$$= A \left| \frac{1}{RCj\omega + 1} \right| e^{j\theta + \angle 1/(RCj\omega + 1)}$$

Find the final time domain solution

$$v_C(t) = A \left| \frac{1}{RCj\omega + 1} \right| \cos(\omega t + \theta + \angle 1/(RCj\omega + 1))$$

#### UC San Diego

#### What does it all mean?

- ◆ The phasor method is built upon the foundations of LTI systems
- When you use phasors, you are exploiting the property that complex sinusoids are eigenfunctions of LTI
- ◆ RLC circuits have real-valued components, which ensures the conjugate symmetry of the frequency response
- ◆ This makes it possible to connect input and output cosines

#### **Connections back to ECE 45**

Lectures 2 - 3 working with signals



Lectures 4 - 7 LTI systems in the time domain

Lectures 11-12 LTI systems in the frequency domain



Lectures 8 - 10 Fourier series

Lectures 13 - 17 Fourier transform



#### **Continuous-time Fourier series**

#### Learning objectives

- Explain the key idea of Fourier series representation of signals
- Specialize the Fourier series to real signals

## Fourier series for CT periodic signals

- Consider the periodic signal x(t) with period T: x(t+T) = x(t)
- lacktriangle The Fourier series representation of the periodic signal x(t) is

$$x(t)=\sum_{k=-\infty}^\infty a_k e^{jk\omega_0 t}$$
 where  $\omega_0=\frac{2\pi}{T}$  is the fundamental frequency

- lacktriangle The Fourier series coefficients of x(t) are  $\{a_k\}$  and  $a_0$  is DC
- lacktriangle The k-th harmonic components of x(t) are  $a_k$  and  $a_{-k}$

### Interpreting the Fourier series

◆ Can represent (most) periodic signals as

$$x(t) = \underbrace{a_0}_{\text{DC offset}} + \underbrace{a_1 e^{j\omega_0 t} + a_{-1} e^{-j\omega_0 t}}_{1^{st} \text{ harmonic on fundamental term}} + \underbrace{a_2 e^{j2\omega_0 t} + a_{-2} e^{-j2\omega_0 t}}_{2^{nd} \text{ harmonic, at } 2\omega_0} + \cdots$$

Checking periodicity

$$x(t+T) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0(t+T)}$$

$$= \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t} e^{jk\omega_0 T}$$

$$= x(t)$$

$$e^{jk\omega_0 T} = e^{jk\frac{2\pi}{T}T}$$
$$= e^{jk2\pi}$$
$$= 1$$

#### UC San Diego


### **Example of Fourier series addition**

http://www.intmath.com/fourier-series/fourier-graph-applet.php
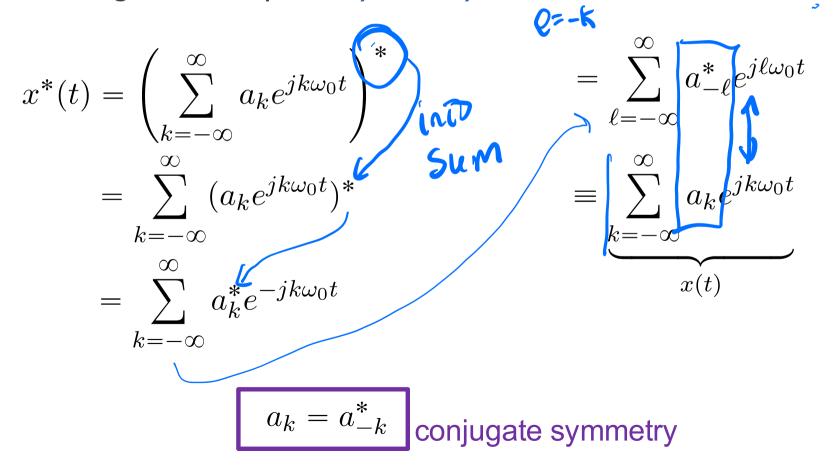
## Special case of real signals

$$x^*(t) = x(t)$$

◆ Real signals have special symmetry in the Fourier series



## Using the symmetry for real signals

◆ Suppose that x(t) is real

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}$$
 is real, which is expected 
$$= a_0 + \sum_{k=1}^{\infty} \left[ a_k e^{jk\omega_0 t} + a_{-k} e^{-jk\omega_0 t} \right]$$
 
$$= a_0 + \sum_{k=1}^{\infty} \left[ a_k e^{jk\omega_0 t} + a_k^* e^{-jk\omega_0 t} \right]$$
 
$$= a_0 + \sum_{k=1}^{\infty} 2\operatorname{Re}\{a_k e^{jk\omega_0 t}\}$$
 
$$z + z^* = 2\operatorname{Re}\{z\}$$

**Decomposition** 

#### UC San Diego

## Writing the coefficients in polar form

• Let  $a_k = A_k e^{j\theta_k}$   $x(t) = a_0 + \sum_{k=1}^{\infty} 2 \mathrm{Re}\{A_k e^{j(k\omega_0 t + \theta_k)}\}$ 



$$= a_0 + 2\sum_{k=1}^{\infty} A_k \cos(k\omega_0 t + \theta_k)$$

Write real signals as a sum of phase shifted cosines and DC term

#### UC San Diego

## Writing the coefficients in Cartesian form



• Let 
$$a_k = B_k + jC_k$$

$$x(t) = a_0 + \sum_{k=1}^{\infty} 2\operatorname{Re}\{a_k e^{jk\omega_0 t}\}$$

$$= a_0 + \sum_{k=1}^{\infty} 2\operatorname{Re}\{(B_k + jC_k)(\cos k\omega_0 t + j\sin k\omega t)\}$$

$$= a_0 + \sum_{k=1}^{\infty} 2(B_k \cos(k\omega_0 t) - C_k \sin(k\omega_0 t))$$

♦ Write real signals as a sum of sine, cosine, and DC term

### Example 4

lacktriangle A CT Periodic & real signal x(t) has a fundamental period T=8. The non-zero Fourier series coefficients (crt)

$$a_1 = a_{-1} = 2$$
 $a_3 = a_{-3} = 4j$ 
 $a_3 = a_{-3} = 4j$ 
 $a_3 = a_{-3} = 4j$ 

• Express 
$$x(t)$$
n exponential, polar and Cartesian forms
$$x(t) = 2 \quad \text{a.e.} \quad \text{i.e.} \quad \text{w.t.} \quad \text{t.e.} \quad \text{w.t.} \quad \text{w.t.} \quad \text{t.e.} \quad \text{w.t.} \quad \text{w.t.} \quad \text{w.t.} \quad \text{w.t.} \quad \text{w.t.$$

### **Example 4 - solution**

## Summary of Fourier series for CT periodic signals

General form of the Fourier series is

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{(j_{k!})t}$$

where 
$$\omega_0 = \frac{2\pi}{T}$$
 is the fundamental frequency

Special forms for when signal is real


$$x(t) = a_0 + 2\sum_{k=1}^{\infty} A_k \cos(k\omega_0 t + \theta_k)$$

$$x(t) = a_0 + \sum_{k=1}^{\infty} 2(B_k \cos(k\omega_0 t) - C_k \sin(k\omega_0 t))$$

## Fourier analysis and orthogonality
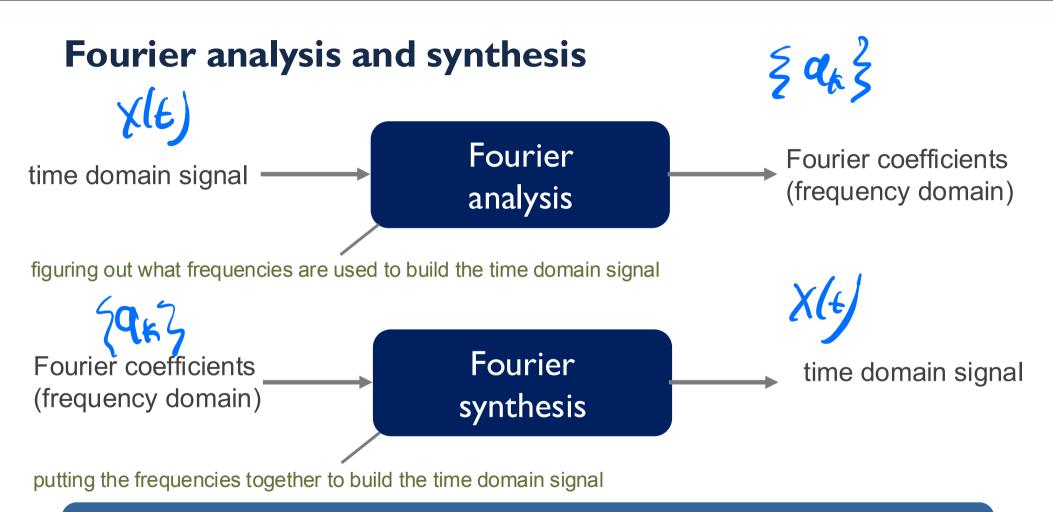
#### Learning objectives

- Connect Fourier series to the inner product of a vector
- Prove orthogonality of complex sinusoids



Fourier theory involves decomposing signals into their Fourier coefficients and building signals from Fourier coefficients

## **Key Fourier equations**





#### Finding the coefficients: Use the analysis equation

$$a_k = \frac{1}{T} \int_T x(t)e^{-jkw_0t}\mathrm{d}t = \frac{1}{T} \int_T x(t)e^{-jk\frac{2\pi}{T}t}\mathrm{d}t$$
 Integrate over the fundamental period T

#### Reconstructing the signal: Use the synthesis equations

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t} = \sum_{k=-\infty}^{\infty} a_k e^{jk\frac{2\pi}{T}t}$$
coefficients complex sinusoid


Signal x(t) that is periodic with fundamental period T

### The analysis equation as an inner product

◆ Inner product of a pair of vectors



$$\mathbf{x}^*\mathbf{y} = \|\mathbf{x}\| \|\mathbf{y}\| \cos(\theta)$$

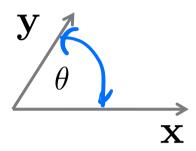

• Inner product between a pair of periodic functions x(t) and y(t)


$$\langle x(t), y(t) \rangle = \int_0^T x(t)y^*(t)dt$$

Way to define magnitude and extent of overlap

## **Orthogonality**

◆ A pair of vectors are orthogonal if

$$\langle \mathbf{x}, \mathbf{y} \rangle = \mathbf{x}^* \mathbf{y} = \|\mathbf{x}\| \|\mathbf{y}\| \cos(\theta) = 0$$

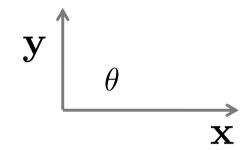

lacktriangle Two periodic functions x(t) and y(t) are orthogonal if

$$\langle x(t), y(t) \rangle = \int_0^T x(t)y^*(t)dt = 0$$

## **Orthogonality of complex sinusoids**



Consider the following periodic signals

The following periodic signals 
$$x(t) = e^{jk\omega_0} \qquad y(t) = e^{jn\omega_0}$$

◆ Compute the inner product between these two signals


$$\int_{0}^{T} e^{j(k-n)\omega_{0}t} dt = \int_{0}^{T} \cos((k-n)\omega_{0}t) + j\sin((k-n)\omega_{0}t) dt$$

$$\times (c)y^{*}(4) = \begin{cases} T & k=n \\ 0 & k \neq n \end{cases}$$

$$T\delta[k-n]$$

Complex sinusoids comprised of different harmonics of the fundamental frequency are orthogonal
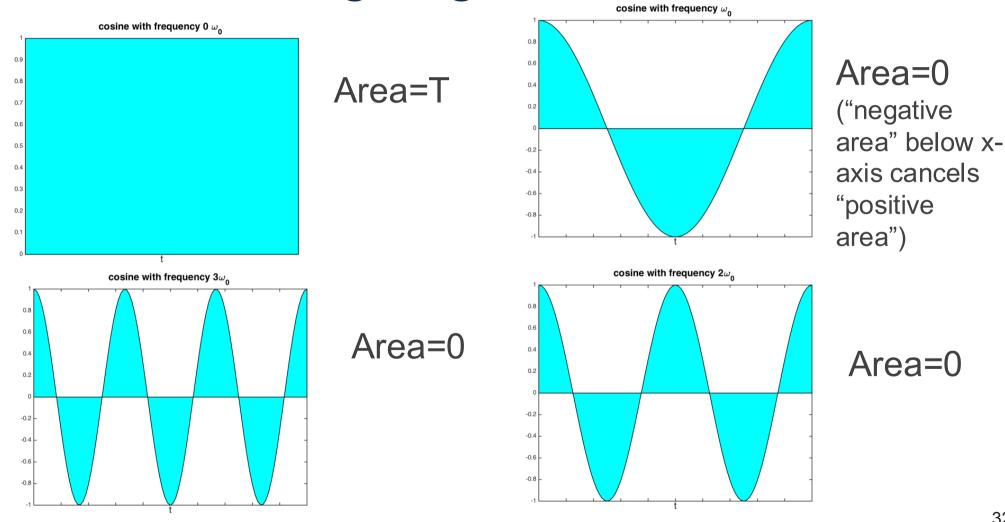
### Illustration of integrating the cosine



### Use orthogonality to check analysis & synthesis

Inserting the synthesis into the analysis equations

$$a_n = \frac{1}{T} \int_0^T x(t)e^{-jn\omega_0 t} dt = \frac{1}{T} \int_0^T \sum_{k=-\infty}^\infty a_k e^{jk\omega_0 t} e^{-jn\omega_0 t} dt$$

$$= \frac{1}{T} \sum_{k=-\infty}^\infty \int_0^T a_k e^{jk\omega_0 t} e^{-jn\omega_0 t} dt$$

$$= \sum_{k=-\infty}^\infty a_k \frac{1}{T} \int_0^T e^{j(k-n)\omega_0 t} dt$$

◆ Note: Assumes the order of integration & sum can be exchanged which is not always the case, relates to discussion in next lecture

### Summary of finding the Fourier series coefficients

◆ The Fourier series coefficients are computed from

$$a_k = \frac{1}{T} \int_T x(t) e^{-j k! \, 0} dt$$

◆ The signal is reconstructed from its coefficients using

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t} = \sum_{k=-\infty}^{\infty} a_k e^{jk\frac{2\pi}{T}t}$$

lacktriangle The Fourier coefficients give insight into "how much" of the frequency  $k\omega_0$  is contained in the signal

## Fourier coefficients of a rectangular pulse train

#### Learning objectives


- Find the Fourier series coefficients of a classic example
- Use the results of this derivation in future lectures

This is an important reference example. It may not be covered in class. We will use the general result though in other example problems as this is an interesting and relevant signal used in circuits.

◆ Find the Fourier series coefficients of the unit pulse train

$$x(t) = egin{cases} 1, & |t| < rac{1}{2} \ 0, & rac{1}{2} < |t| < rac{7}{2} \end{cases}$$

and is repeated every  ${\cal T}$ 

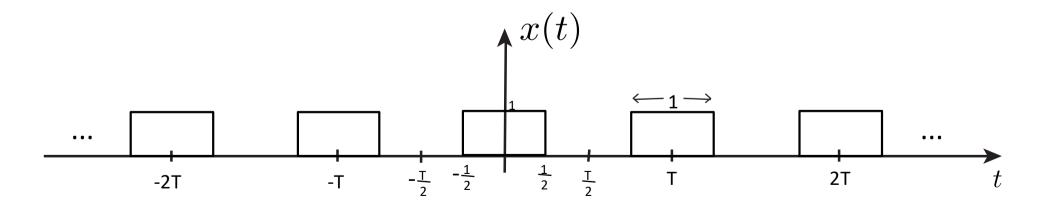

$$a_{k} = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} x(t)e^{-jk\omega_{0}t}dt, \quad \omega_{0} = \frac{2\pi}{T}$$

$$= \frac{1}{T} \int_{-\frac{1}{2}}^{\frac{1}{2}} 1 \cdot e^{-jk\omega_{0}t}dt$$

$$= \frac{-1}{jk\omega_{0}T} e^{-jk\omega_{0}t} \Big|_{-\frac{1}{2}}^{\frac{1}{2}}$$

$$= -\frac{1}{jk\omega_{0}T} \left( e^{\frac{-jk\omega_{0}}{2}} - e^{\frac{jk\omega_{0}}{2}} \right)$$

$$= \frac{2}{k\omega_{0}T} \frac{1}{2j} \left( e^{\frac{jk\omega_{0}}{2}} - e^{-\frac{jk\omega_{0}}{2}} \right)$$


$$a_k = \frac{1}{T} \frac{\sin\left(\frac{k\omega_0}{2}\right)}{\frac{k\omega_0}{2}}$$

$$= \frac{1}{T} \frac{\sin\left(\pi \frac{k\omega_0}{2\pi}\right)}{\pi \frac{k\omega_0}{2\pi}}$$

$$= \frac{1}{T} \operatorname{sinc}\left(\frac{k\omega_0}{2\pi}\right)$$
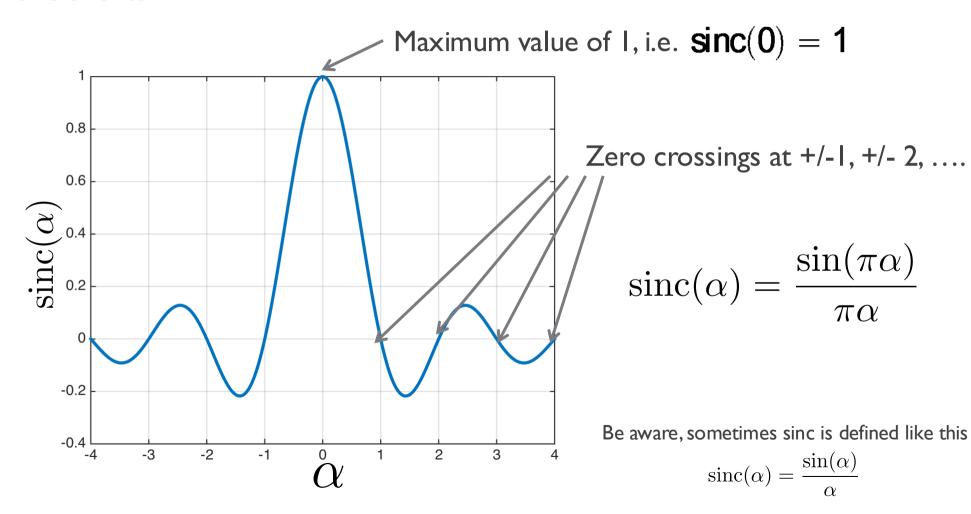
#### We define the sinc as

$$\operatorname{sinc}(x) = \frac{\sin(\pi x)}{\pi x}$$



 $\bullet$  What about k = 0?

$$a_0 = \frac{1}{T} \int_{-\frac{1}{2}}^{\frac{1}{2}} \underbrace{x(t)}_{1} dt = \frac{1}{T} \left( \frac{1}{2} - \left( -\frac{1}{2} \right) \right) = \frac{1}{T}$$

◆ As an side, for the sinc function


$$\lim_{t \to \infty} \frac{\sin(\pi t)}{\pi t} = \lim_{t \to \infty} \frac{\pi \cos(\pi t)}{\pi} = 1$$

◆ Therefore the following holds for all values of k

$$a_k = \frac{1}{T} \operatorname{sinc}\left(\frac{k\omega_0}{2\pi}\right) = \frac{\omega_0}{2\pi} \operatorname{sinc}\left(\frac{k\omega_0}{2\pi}\right)$$

## Example with T=2


#### Pulse train 6

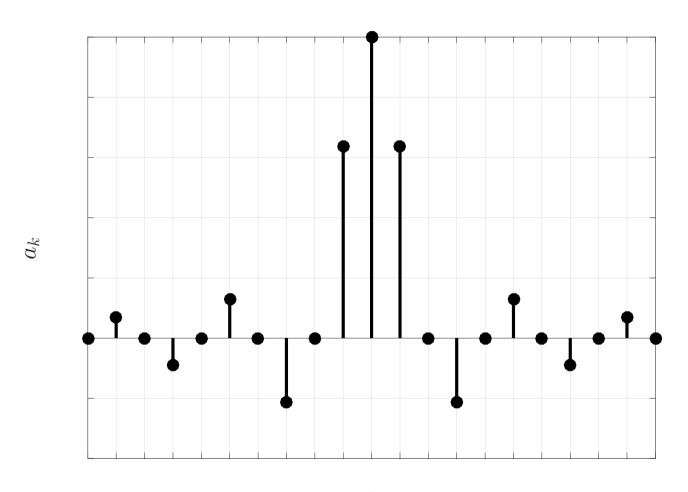

#### UC San Diego



#### From O&W Example 3.5

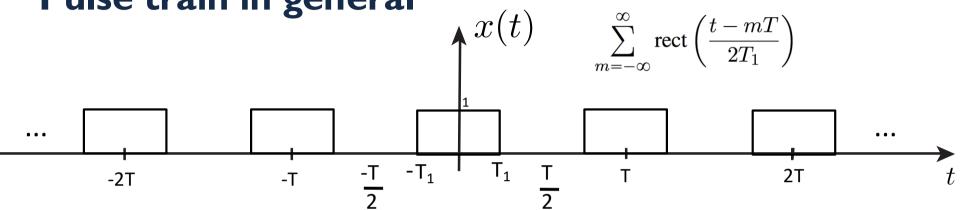

#### From the book

$$a_k = \frac{\sin\left(\pi k \frac{2T_1}{T}\right)}{k\pi} \quad k \neq 0$$

$$a_0 = \frac{2T_1}{T}$$

# Rewritten using the sinc function $sinc(x) = \frac{sin(\pi x)}{\pi x}$

$$a_k = \frac{\omega_0 T_1}{\pi} \operatorname{sinc}\left(\frac{k\omega_0 T_1}{\pi}\right)$$

with fundamental frequency

$$a_k = \frac{2T_1}{T} \operatorname{sinc}\left(\frac{k2T_1}{T}\right)$$

simplified